

Date: 17/3/21

Experiment no. 3



Objective: To study simulation of half wave rectifier using diodes

Software used: Multisim Live



Theory: Rectifier changes AC to DC and it is an essential part of power supply. The unique property of a diode, permitting the current to flow in one direction, is utilised in rectifiers.

Circuit diagram:

1. Half wave rectifier without filter

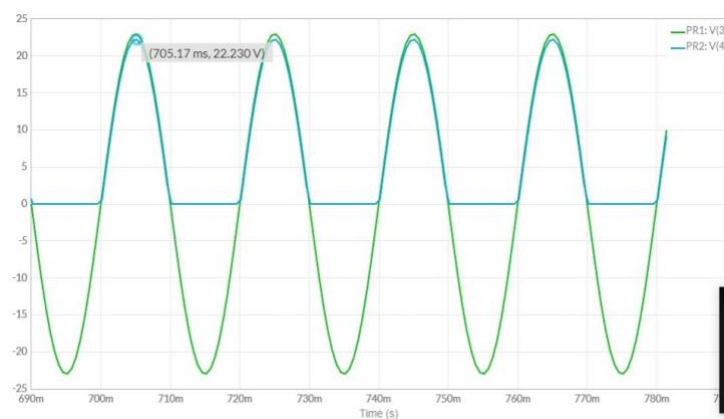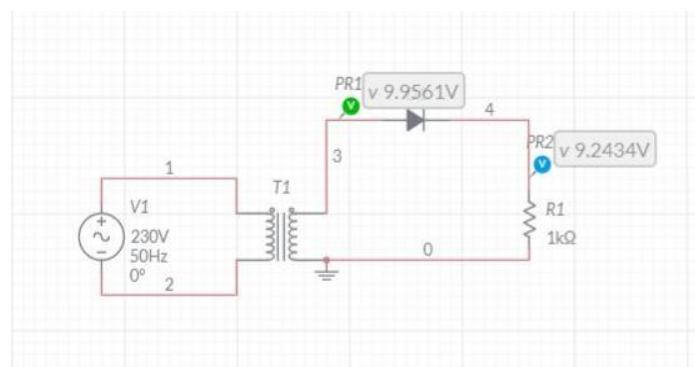

2. Half wave rectifier with filter

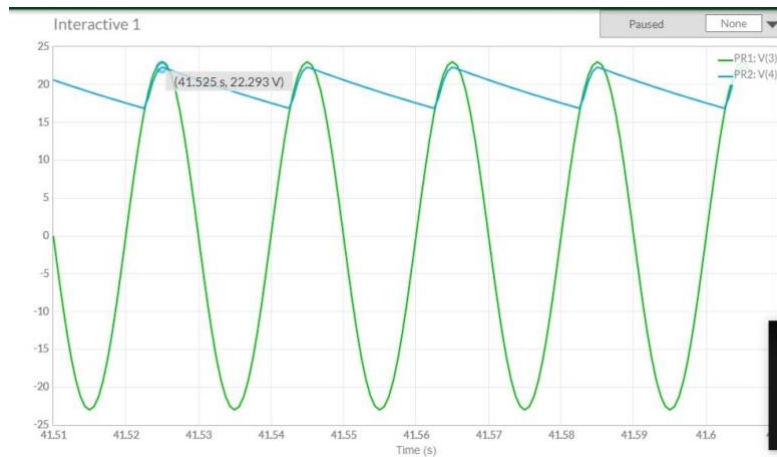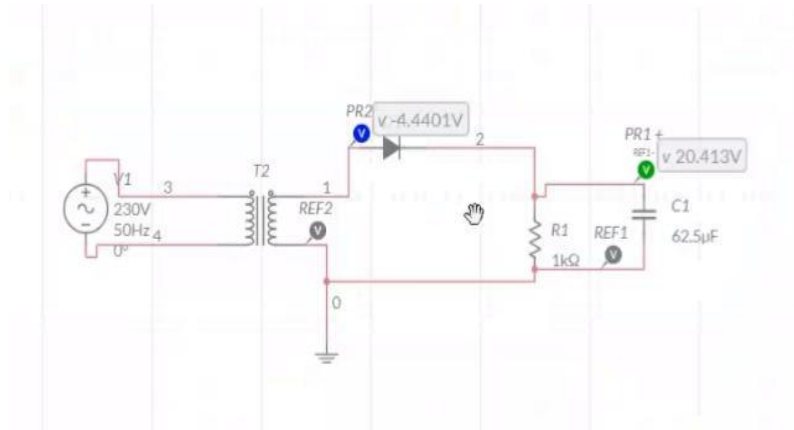

Results & observations:

Observations:





1. Half wave rectifier without filter

V_{p-p}	$V_p = V_{p-p}/2$	$V_{rms} = V_p/2^{1/2}$
22.230V	11.115V	7.859V

2. Half wave rectifier with filter

V_{p-p}	$V_p = V_{p-p}/2$	$V_{rms} = V_p/2^{1/2}$
22.293V	11.1465V	7.881V

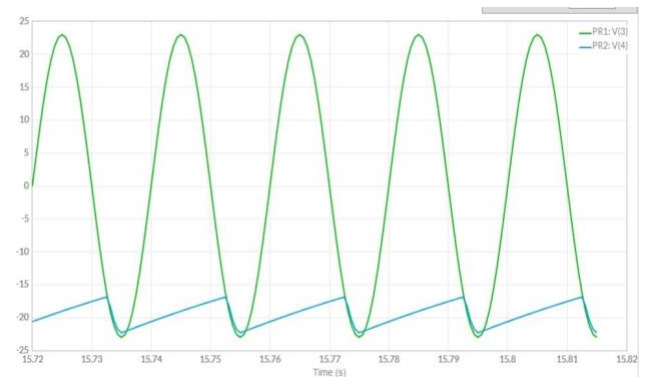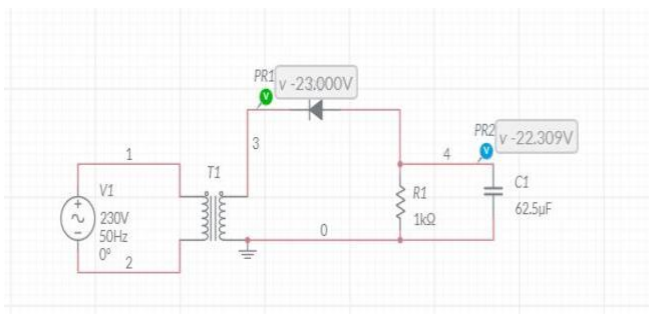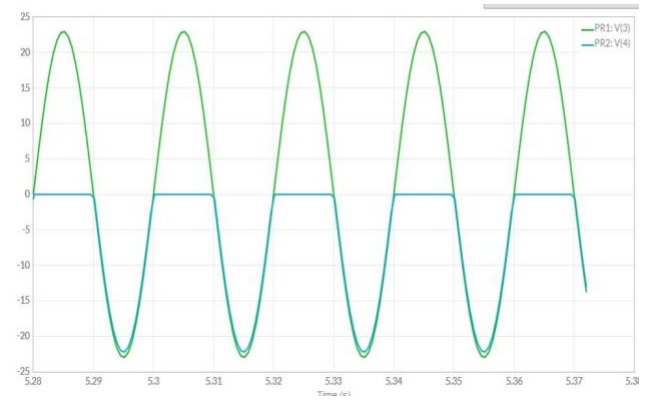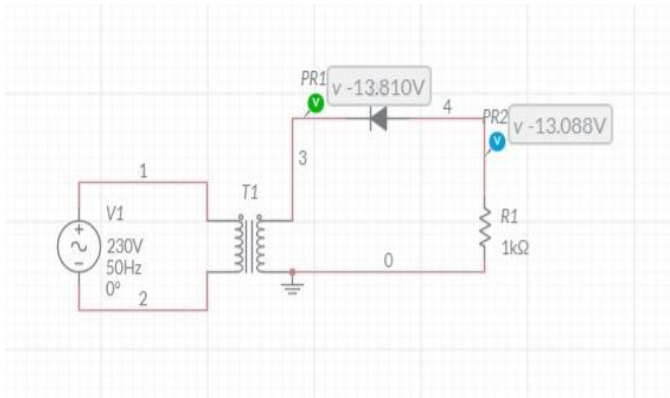If we change the direction of diode in Half wave rectifier circuit with filter and without filter then output voltage becomes negative



Result: The Graphs, Diagrams and observations show us the simulation of half wave rectifier using diodes

Submitted by: G Hruthesh reddy (20BCB7031)